


IF




ID

EXE

MEM

WB

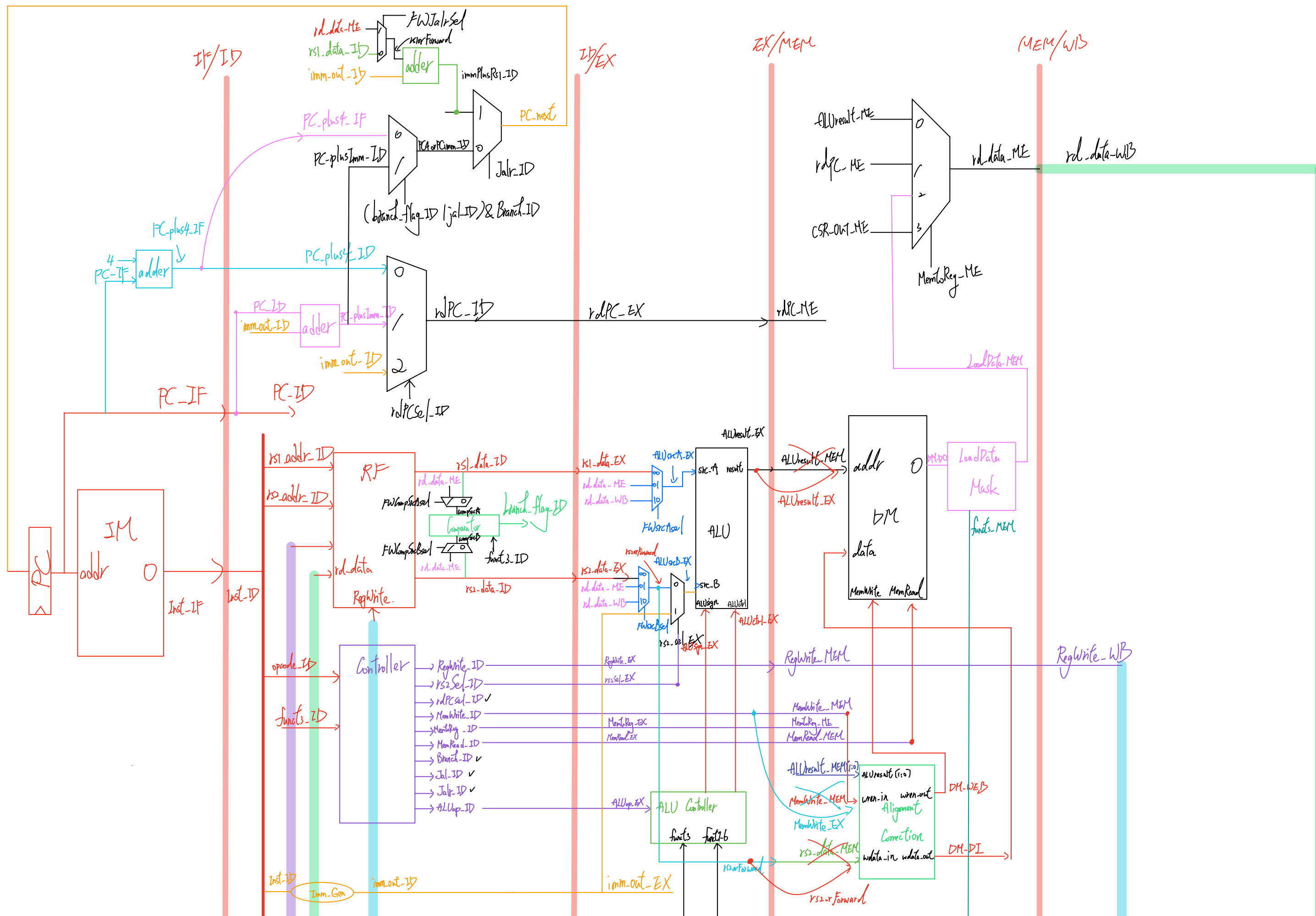

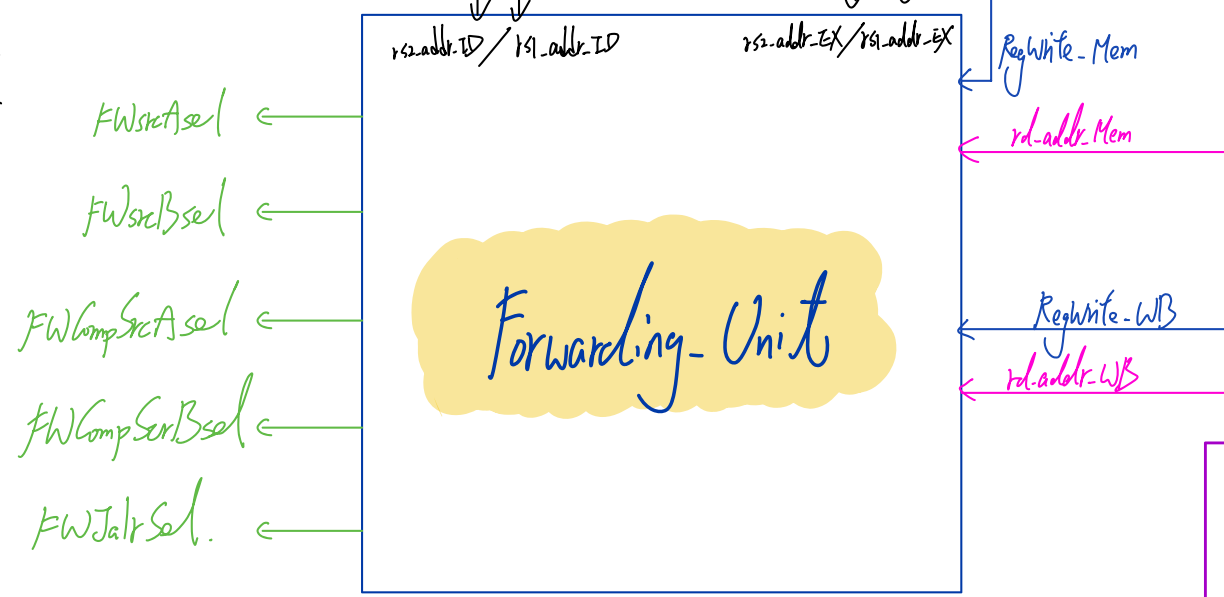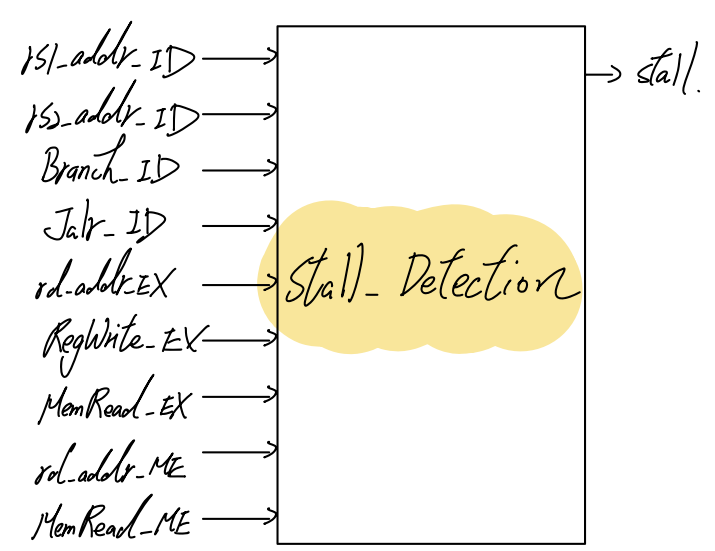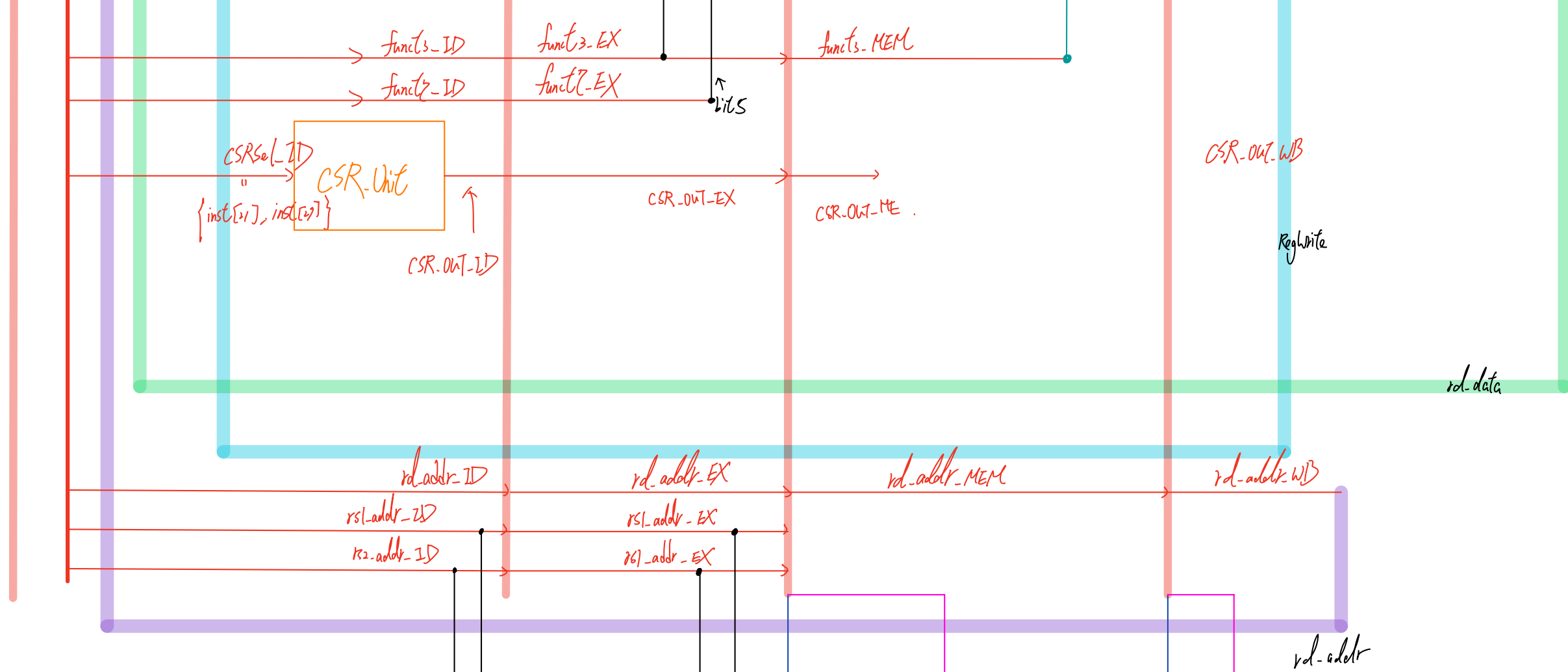


Note: 若 WB stage 要寫回 rd 時, 剛好有指令 read rd, 則會來不及, 可以讓 RF 的輸出-輸入來解決須等待 - cycle 的問題!

DM 有 delay 輸出, 對應 policy:

- 1: 將 $addr$ 提早一個 cycle 給, $data$ 會與沒有 delay 的 DM 同時出來.
- 2: 因為會影響到寫入時序, 因此也將寫入 $data$ & $write_enable$ 提早給.


$rs2_or_forward$ $MemWrite_EX$

IM 有 one cycle delay 後的改動

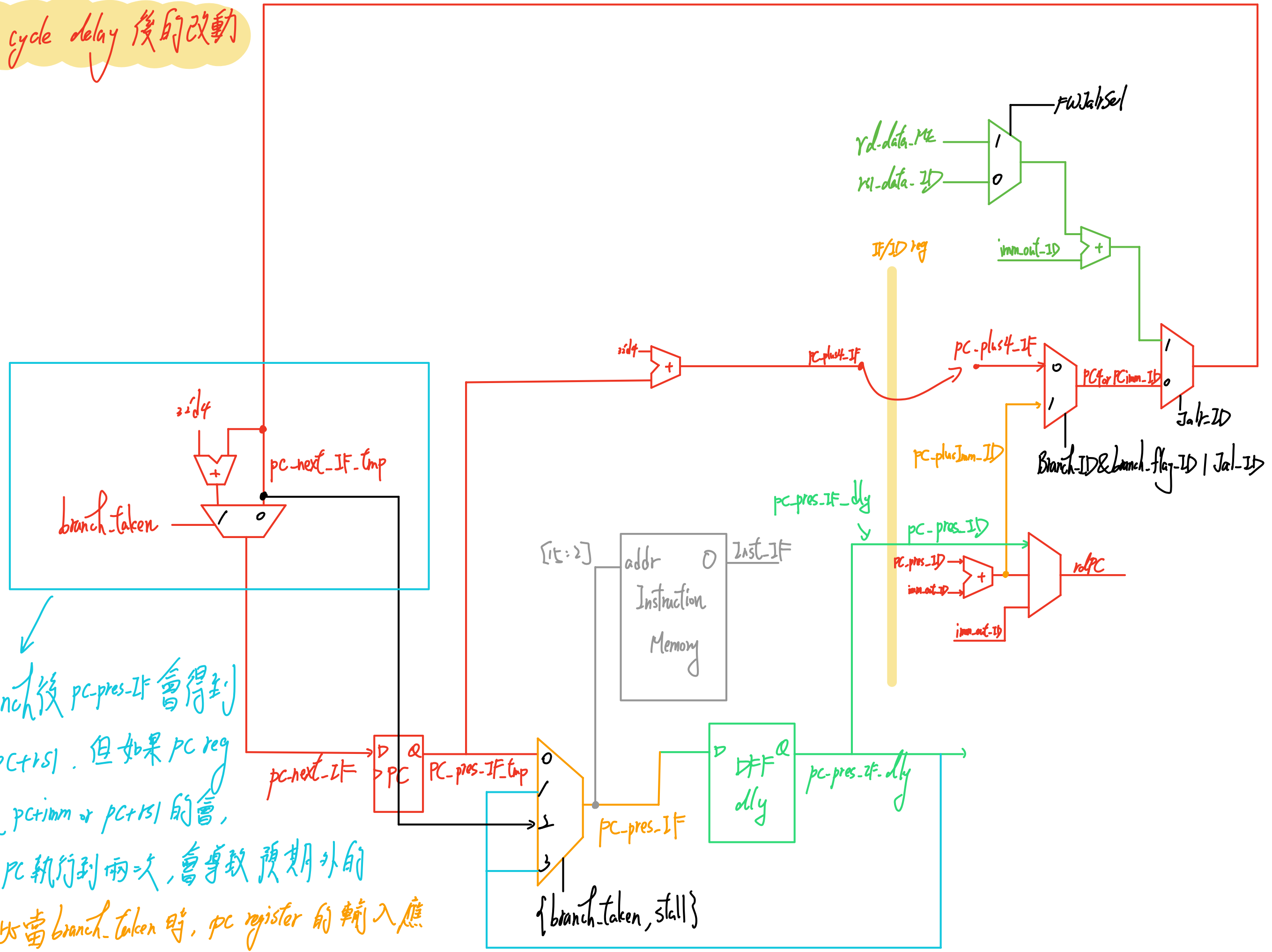

由於在 branch 後 `pc-pres-IF` 會得到 `PC+imm` or `PC+rs1`，但如果 PC reg 的 input 也是 `PC+imm` or `PC+rs1` 的會，會使同一個 PC 執行到兩次，會導致預期外的錯誤，因此當 `branch-taken` 時，PC register 的輸入應為 branch 後的下道指令，也就是 `PC+imm+4` or `PC+rs1+4` ✖

Only forwarding

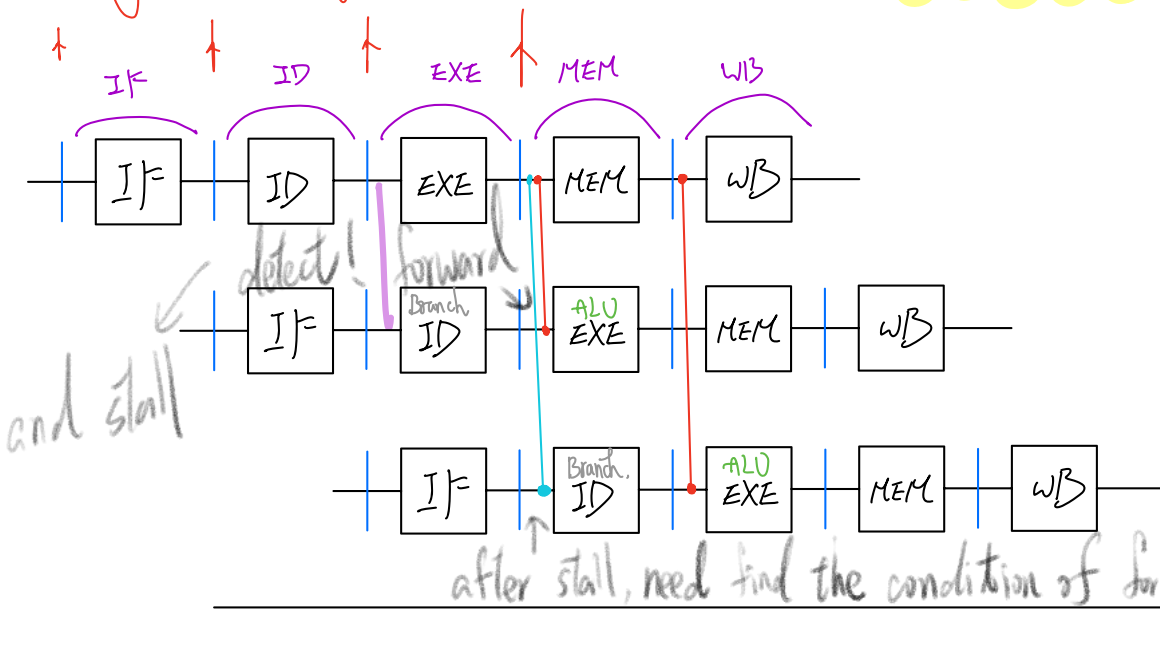

R-R or R-X-R

if (RegWrite-MEM == 1 && rd_addr-MEM != 0)
 if (rd_addr-MEM == rs1_addr-EX) ALUforwarding-srcA = ALUresult-MEM **FWsrcAse1 = 1'b0**
 if (rd_addr-MEM == rs2_addr-EX) ALUforwarding-srcB = ALUresult-MEM **FWsrcBse1 = 1'b0**
 else if (RegWrite-WB == 1 && rd_addr-WB != 0)
 if (rd_addr-WB == rs1_addr-EX) ALUforwarding-srcA = ALUresult-WB **FWsrcAse1 = 1'b10**
 if (rd_addr-WB == rs2_addr-EX) ALUforwarding-srcB = ALUresult-WB **FWsrcBse1 = 1'b10**

因為ID才decode出來，所以上一條用EX去寫。

R-Branch


need to stall for one cycle,
mind the flush!!

stall 1 cycle & forwarding

if (RegWrite-MEM == 1 && rd_addr-MEM != 0) {
 if (rd_addr-MEM == rs1_addr-ID) **FWCompSrcAse1 = ALUresult-MEM**
 if (rd_addr-MEM == rs2_addr-ID) **FWCompSrcBse1 = ALUresult-MEM**
}

if (RegWrite-EX == 1 && (Branch-ID | Jalr-ID)) {
 if (rd_addr-EX == rs1_addr-ID || rd_addr-EX == rs2_addr-ID)
 stall = 1
 else
 stall = 0
}

Load-R => need stall one cycle.

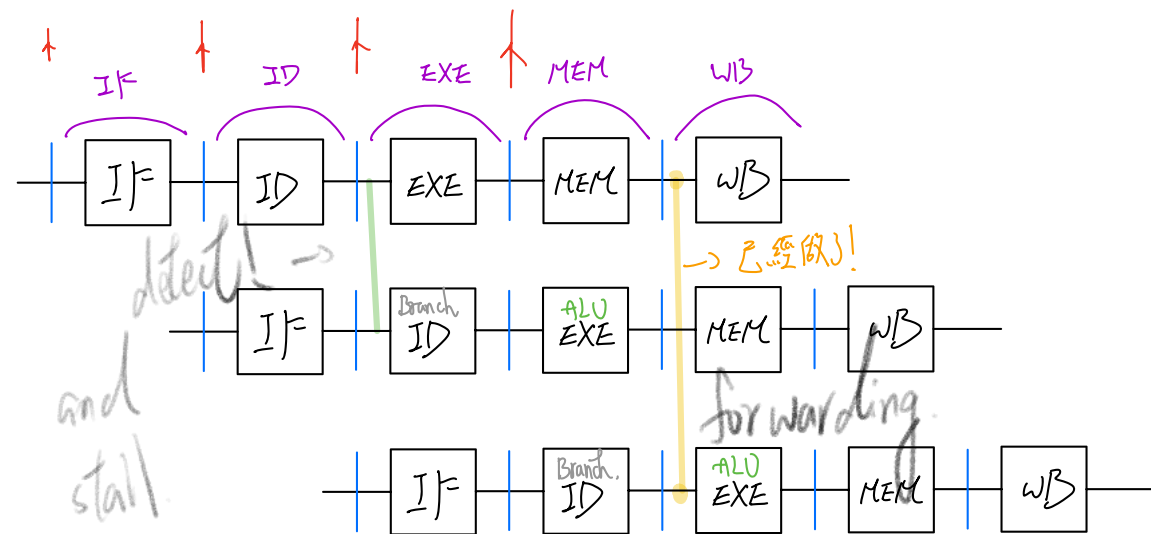


if (MemRead-EX == 1 && RegWrite-EX == 1) {
 if (rd_addr-EX == rs1_addr-ID || rd_addr-EX == rs2_addr-ID)
 stall = 1
 else
 stall = 0
}

Same.

stall 1 cycle & forwarding.

Load-Branch.

Load

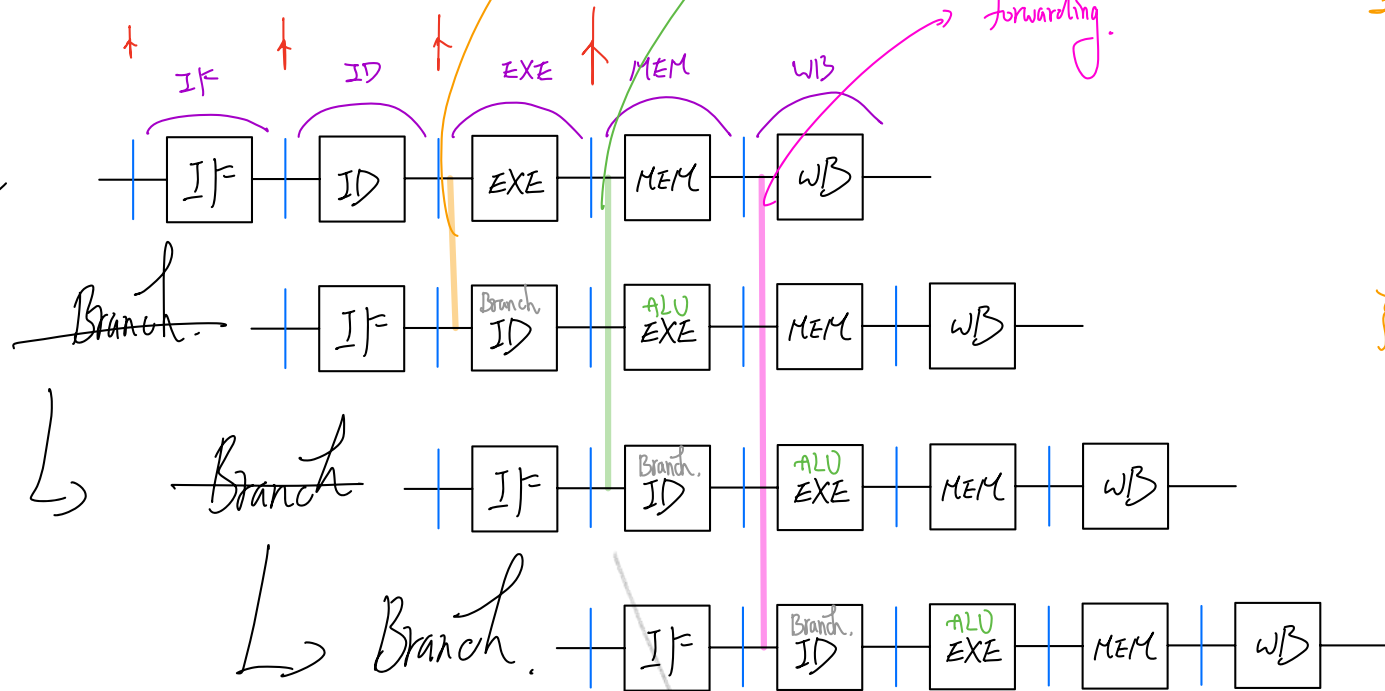

already forwarding in other condition (R-R, R-B)

stall first time.

```

if (memRead-EX == 1 && RegWrite-EX == 1) {
    if (rd-addr-EX == rs1-addr-ID || rd-addr-EX == rs2-addr-ID)
        stall = 1;
    else
        stall = 0;
}
    
```

stall second time.

```

if (memRead-MEM == 1 && (Branch-ID | Jalr-ID)) {
    if (rd-addr-MEM == rs1-addr-ID || rd-addr-MEM == rs2-addr-ID)
        stall = 1;
    else
        stall = 0;
}
    
```

~~X~~